

# Digital Signal Processing

## EE3900

M Avinash  
AI21BTECH11018

November 2, 2022

### CONTENTS

#### 1. DEFINITIONS

1. The unit step function is

$$u(t) = \begin{cases} 1 & t > 0 \\ \frac{1}{2} & t = 0 \\ 0 & t < 0 \end{cases} \quad (1.1)$$

2. The Laplace transform of  $g(t)$  is defined as

$$G(s) = \int_{-\infty}^{\infty} g(t)e^{-st} dt \quad (1.2)$$

#### 2. LAPLACE TRANSFORM

1. In the circuit, the switch S is connected to position P for a long time so that the charge on the capacitor becomes  $q_1 \mu C$ . Then S is switched to position Q. After a long time, the charge on the capacitor is  $q_2 \mu C$ .

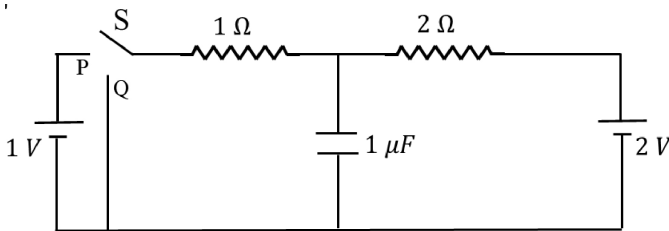


Fig. 2.1.

2. Draw the circuit using latex-tikz.

**Solution:** The following code yields Fig.??

```
wget https://github.com/AvinashNayak27/
Spice/blob/master/Tikz%20Circuits/2.2.tex
```

3. Find  $q_1$ .

**Solution:** Before switching S to Q: At steady state, which achieved when switch S is at P

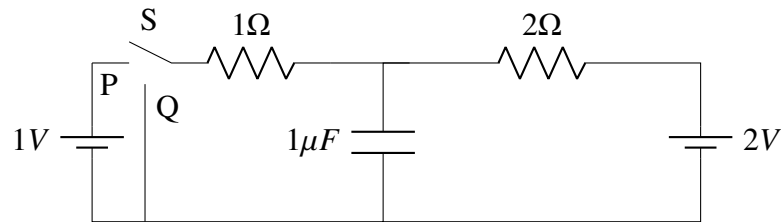


Fig. 2.2. Given Circuit

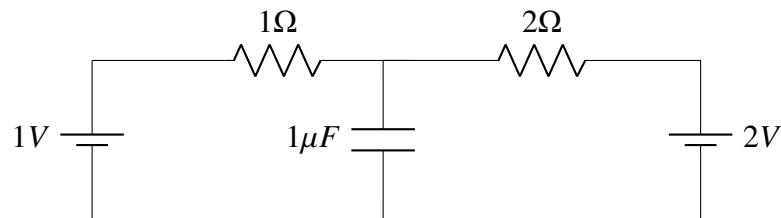


Fig. 2.3. Before switching S to Q

for long time capacitor behaves as an open switch, hence current through capacitor is 0, Let  $i$  be the current flowing in the circuit at steady state. Applying KVL ,

$$1 - i - 2i - 2 = 0 \quad (2.1)$$

$$3i = -1 \Rightarrow i = \frac{-1}{3} A \quad (2.2)$$

Potential Difference across the capacitor at steady state is

$$1 - \left( \frac{-1}{3} \right) = \frac{4}{3} V \quad (2.3)$$

$$q_1 = \frac{4}{3} \cdot 1 \quad (2.4)$$

$$= \frac{4}{3} \mu C \quad (2.5)$$

4. Show that the Laplace transform of  $u(t)$  is  $\frac{1}{s}$  and find the ROC.

**Solution:** We know that Laplace Transform of function  $f(t)$  is given as  $F(s)$ ,

$$F(s) = \int_0^{\infty} f(t)e^{-st} dt \quad (2.6)$$

$$(2.7)$$

For  $u(t)$ , we have,

$$F(s) = \int_0^{\infty} u(t)e^{-st} dt \quad (2.8)$$

Using (??),

$$F(s) = \int_0^{\infty} u(t)e^{-st} dt \quad (2.9)$$

$$= \int_0^{\infty} e^{-st} dt \quad (2.10)$$

$$= -\left(0 - \frac{1}{s}\right) \quad (2.11)$$

$$= \frac{1}{s} \quad (2.12)$$

ROC is  $Re(s) > 0$  since for  $s > 0$ ,  $e^{-st} < \infty$  for  $t \rightarrow \infty$

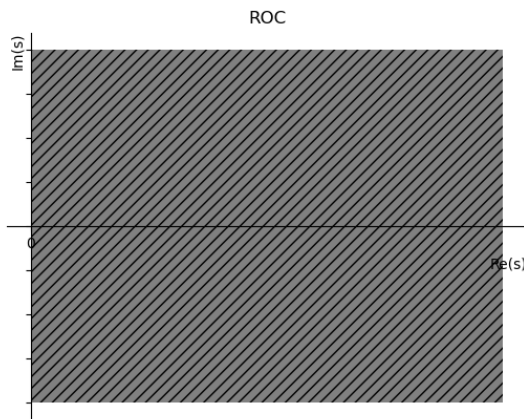


Fig. 2.4.

5. Show that

$$e^{-at}u(t) \xleftrightarrow{\mathcal{L}} \frac{1}{s+a}, \quad a > 0 \quad (2.13)$$

and find the ROC.

**Solution:** From ??,

$$F(s) = \int_0^{\infty} u(t)e^{-at}e^{-st} dt \quad (2.14)$$

$$= \int_0^{\infty} u(t)e^{-(s+a)t} dt \quad (2.15)$$

$$= \int_0^{\infty} e^{-(s+a)t} dt \quad (2.16)$$

$$= -\left(0 - \frac{1}{s+a}\right) \quad (2.17)$$

$$= \frac{1}{s+a} \quad (2.18)$$

ROC is

$$Re(s) + a > 0 \Rightarrow Re(s) > -a \quad (2.19)$$

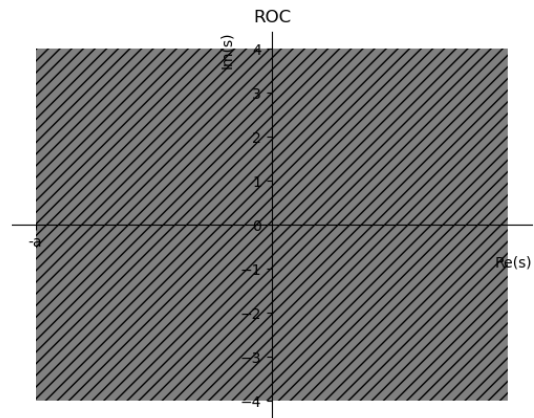


Fig. 2.5.

6. Now consider the following resistive circuit transformed from Fig. ?? where

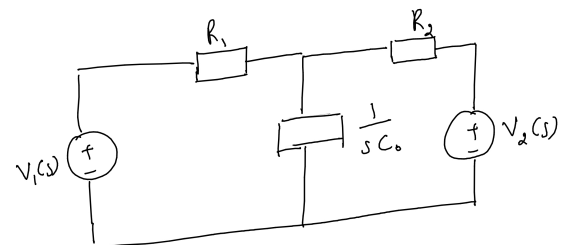


Fig. 2.6.

$$u(t) \xrightarrow{\mathcal{L}} V_1(s) \quad (2.20)$$

$$2u(t) \xrightarrow{\mathcal{L}} V_2(s) \quad (2.21)$$

Find the voltage across the capacitor  $V_{C_0}(s)$ .

**Solution:**

$$R_{eff} = \frac{1}{1 + \frac{1}{2}} = \frac{2}{3} \Omega \quad (2.22)$$

$$V_{eff} = \frac{1}{1 + \frac{1}{2}} = \frac{2}{3} V \quad (2.23)$$

$$V_{C_0}(s) = V_S(s) \frac{C_0}{C_0 + R_{eff}} \quad (2.24)$$

$$= \left( \frac{4}{3s} \right) \left( \frac{\frac{1}{s}}{\frac{1}{s} + \frac{2}{3}} \right) \quad (2.25)$$

$$= \frac{3 + 4s}{3s \left( s + \frac{3}{2} \right)} \quad (2.26)$$

7. Find  $v_{C_0}(t)$ . Plot using python.

**Solution:** Running the following code gives the plot.

```
wget https://github.com/AvinashNayak27/
Spice/blob/master/codes/2.7.py
```

Using (??),

$$\frac{3 + 4s}{3s \left( s + \frac{3}{2} \right)} = \frac{2}{3s} + \frac{2}{3 \left( \frac{3}{2} + s \right)} \quad (2.27)$$

Apply inverse Laplacian Transform,

$$V_{C_0}(s) \xrightarrow{\mathcal{L}^{-1}} V_{C_0}(t) \quad (2.28)$$

$$\mathcal{L}^{-1} [V_{C_0}(s)] = \mathcal{L}^{-1} \left[ \frac{2}{3s} + \frac{2}{3 \left( \frac{3}{2} + s \right)} \right] \quad (2.29)$$

$$= \mathcal{L}^{-1} \left[ \frac{2}{3s} \right] - \frac{2}{3} \mathcal{L}^{-1} \left[ \frac{1}{\frac{3}{2} + s} \right] \quad (2.30)$$

Since,

$$\mathcal{L}^{-1} \left[ \frac{1}{s} \right] = u(t) \quad (2.31)$$

$$\mathcal{L}^{-1} \left[ \frac{1}{s - a} \right] = e^{at} u(t) \quad (2.32)$$

Using the above equations,

$$V_{C_0}(t) = \frac{2}{3} \left( 1 + e^{-\frac{3}{2}t} \right) u(t) \quad (2.33)$$

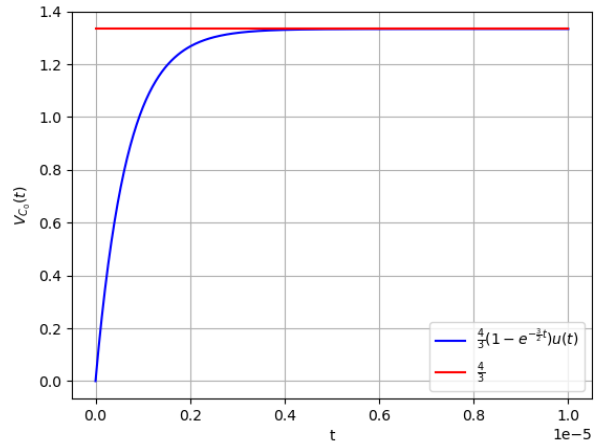


Fig. 2.7. Plot of  $V_{C_0}(t)$

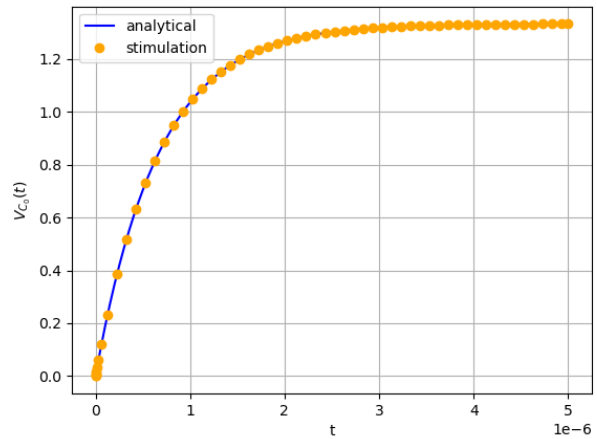


Fig. 2.8.

8. Verify your result using ngspice.

**Solution:**

9. Obtain Fig. ?? using the equivalent differential equation

**Solution:** Results obtained can be verified by running the following code.

```
wget https://github.com/AvinashNayak27/
Spice/blob/master/codes/2.8.cir
```

And is plotted using the below code.

```
wget https://github.com/AvinashNayak27/
Spice/blob/master/codes/2.8.py
```

Using Kirchoff's junction law

$$\frac{v_c(t) - v_1(t)}{R_1} + \frac{v_c(t) - v_2(t)}{R_2} + \frac{dq}{dt} = 0 \quad (2.34)$$

where  $q(t)$  is the charge on the capacitor  
On taking the Laplace transform on both sides of this equation

$$\frac{V_c(s) - V_1(s)}{R_1} + \frac{V_c(s) - V_2(s)}{R_2} + (sQ(s) - q(0^-)) = 0 \quad (2.35)$$

But  $q(0^-) = 0$  and

$$q(t) = C_0 v_c(t) \quad (2.36)$$

$$\Rightarrow Q(s) = C_0 V_c(s) \quad (2.37)$$

Thus

$$\frac{V_c(s) - V_1(s)}{R_1} + \frac{V_c(s) - V_2(s)}{R_2} + sC_0 V_c(s) = 0 \quad (2.38)$$

$$\Rightarrow \frac{V_c(s) - V_1(s)}{R_1} + \frac{V_c(s) - V_2(s)}{R_2} + \frac{V_c(s) - 0}{\frac{1}{sC_0}} = 0 \quad (2.39)$$

which is the same equation as the one we obtained from Fig. ??

### 3. INITIAL CONDITIONS

1. Find  $q_2$  in Fig. ??.

**Solution:** At steady state capacitor behaves as an open switch. Hence  $V_{C_0} = V_{1\Omega}$ .

Let  $i$  be the current in the circuit. Using KVL,

$$2 - 2i - i = 0 \Rightarrow i = \frac{2}{3} \quad (3.1)$$

$$V_{1\Omega} = i \times 1 = \frac{2}{3}V \quad (3.2)$$

$$V_{C_0} = \frac{q_2}{C_0} = V_{1\Omega} = \frac{2}{3} \quad (3.3)$$

$$\Rightarrow q_2 = \frac{2}{3}\mu C \quad (3.4)$$

2. Draw the equivalent  $s$ -domain resistive circuit when S is switched to position Q. Use variables  $R_1, R_2, C_0$  for the passive elements. Use latex-tikz.

**Solution:**

3.  $V_{C_0}(s) = ?$

**Solution:** Let voltage across capacitor be  $V$ . Using KCL at node in Fig. ??

$$\frac{V - 0}{R_1} + \frac{V - \frac{2}{s}}{R_2} + sC_0 \left( V - \frac{4}{3s} \right) = 0 \quad (3.5)$$

$$\Rightarrow V_{C_0}(s) = \frac{\frac{2}{sR_2} + \frac{4C_0}{3}}{\frac{1}{R_1} + \frac{2}{R_2} + sC_0} \quad (3.6)$$

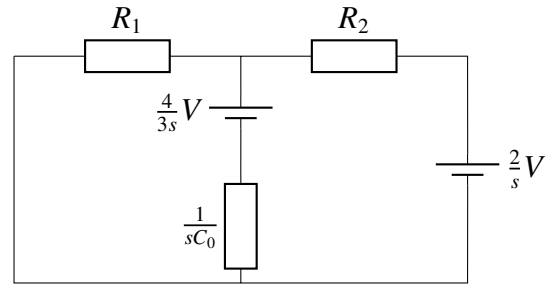


Fig. 3.1. After switching S to Q

4.  $v_{C_0}(t) = ?$  Plot using python.

**Solution:** Running the following code gives the plot.

```
wget https://github.com/AvinashNayak27/
Spice/blob/master/codes/3.4.py
```

From (??),

$$V_{C_0}(s) = \frac{4}{3} \left( \frac{1}{\frac{1}{C_0} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) + s} \right) + \frac{2}{R_2 \left( \frac{1}{R_1} + \frac{1}{R_2} \right)} \left( \frac{1}{s} - \frac{1}{\frac{1}{C_0} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) + s} \right) \quad (3.7)$$

Taking an inverse Laplace Transform,

$$v_{C_0}(t) = \frac{4}{3} e^{-\left(\frac{1}{R_1} + \frac{1}{R_2}\right)\frac{t}{C_0}} u(t) + \frac{2}{R_2 \left( \frac{1}{R_1} + \frac{1}{R_2} \right)} \left( 1 - e^{-\left(\frac{1}{R_1} + \frac{1}{R_2}\right)\frac{t}{C_0}} \right) u(t) \quad (3.8)$$

Substituting values gives

$$v_{C_0}(t) = \frac{2}{3} \left( 1 + e^{-(1.5 \times 10^6)t} \right) u(t) \quad (3.9)$$

5. Verify your result using ngspice.

**Solution:** Results obtained can be verified by running the following code.

```
wget https://github.com/AvinashNayak27/
Spice/blob/master/codes/3.5.cir
```



Running the below code plots the figure ??, and verifies our result.

```
wget https://github.com/AvinashNayak27/
Spice/blob/master/codes/3.5.py
```

6. Find  $v_{C_0}(0^-)$ ,  $v_{C_0}(0^+)$  and  $v_{C_0}(\infty)$ .

**Solution:** From the initial conditions,

$$v_{C_0}(0^-) = \frac{q_1}{C} = \frac{4}{3}V \quad (3.10)$$

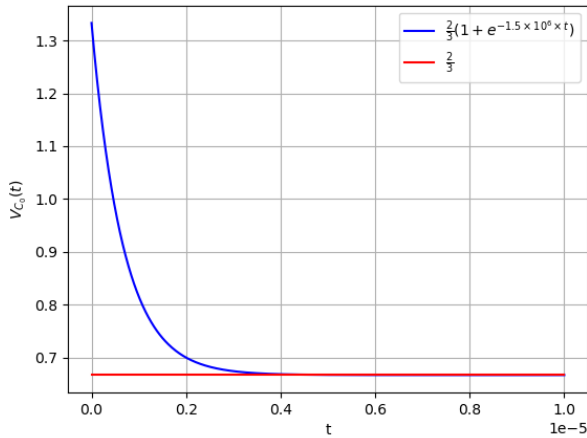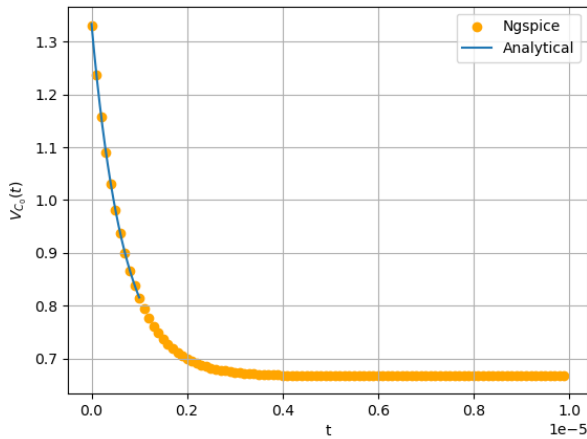Fig. 3.2. Plot of  $V_{C_0}(t)$ Fig. 3.3. ngspice plot of  $V_{C_0}(t)$ 

Using (??),

$$v_{C_0}(0+) = \lim_{t \rightarrow 0+} v_{C_0}(t) = \frac{4}{3}V \quad (3.11)$$

$$v_{C_0}(\infty) = \lim_{t \rightarrow \infty} v_{C_0}(t) = \frac{2}{3}V \quad (3.12)$$

7. Obtain Fig. ?? using the equivalent differential equation

**Solution:** Using Kirchoff's junction law

$$\frac{v_c(t) - 0}{R_1} + \frac{v_c(t) - v_2(t)}{R_2} + \frac{dq}{dt} = 0 \quad (3.13)$$

where  $q(t)$  is the charge on the capacitor. On taking the Laplace transform on both sides of

the equation (??), we get,

$$\frac{V_c(s) - 0}{R_1} + \frac{V_c(s) - V_2(s)}{R_2} + sQ(s) - q(0^-) = 0 \quad (3.14)$$

But  $q(0^-) = \frac{4}{3}C_0$  and

$$q(t) = C_0 v_c(t) \quad (3.15)$$

$$\Rightarrow Q(s) = C_0 V_c(s) \quad (3.16)$$

Thus

$$\frac{V_c(s) - 0}{R_1} + \frac{V_c(s) - V_2(s)}{R_2} + \left( sC_0 V_c(s) - \frac{4}{3}C_0 \right) = 0 \quad (3.17)$$

$$\Rightarrow \frac{V_c(s) - 0}{R_1} + \frac{V_c(s) - V_2(s)}{R_2} + \frac{V_c(s) - \frac{4}{3s}}{\frac{1}{sC_0}} = 0 \quad (3.18)$$

which is the same equation as the one we obtained from Fig. ??

#### 4. BILINEAR TRANSFORM

4.1. In Fig. ??, consider the case when  $S$  is switched to  $Q$  right in the beginning. Formulate the differential equation

**Solution:** The differential equation is the same as before

$$\frac{v_c(t) - 0}{R_1} + \frac{v_c(t) - v_2(t)}{R_2} + \frac{dq}{dt} = 0 \quad (4.1)$$

$$\text{i.e., } \frac{v_c(t)}{R_1} + \frac{v_c(t) - v_2(t)}{R_2} + C_0 \frac{dv_c}{dt} = 0 \quad (4.2)$$

but with a different initial condition

$$q(0^-) = q(0) = 0 \quad (4.3)$$

4.2. Find  $H(s)$  considering the output voltage at the capacitor

**Solution:** On taking the Laplace transform on both sides of this equation

$$\frac{V_c(s)}{R_1} + \frac{V_c(s) - V_2(s)}{R_2} + sQ(s) - 0 = 0 \quad (4.4)$$

$$\Rightarrow V_c(s) \left( \frac{1}{R_1} + \frac{1}{R_2} \right) + sC_0 V_c(s) = \frac{V_2(s)}{R_2} \quad (4.5)$$

$$\Rightarrow \frac{V_c(s)}{V_2(s)} = \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2} + sC_0} \quad (4.6)$$

The transfer function is thus

$$H(s) = \frac{\frac{1}{R_2 C_0}}{s + \frac{1}{R_1 C_0} + \frac{1}{R_2 C_0}} \quad (4.7)$$

On substituting the values, we get

$$H(s) = \frac{5 \times 10^5}{s + 1.5 \times 10^6} \quad (4.8)$$

4.3. Plot  $H(s)$ . What kind of filter is it?

**Solution:** Download the following Python code that plots Fig. ??

```
wget https://github.com/AvinashNayak27/
Spice/blob/master/codes/4.3.py
```

Run the codes by executing

```
python 4.3.py
```

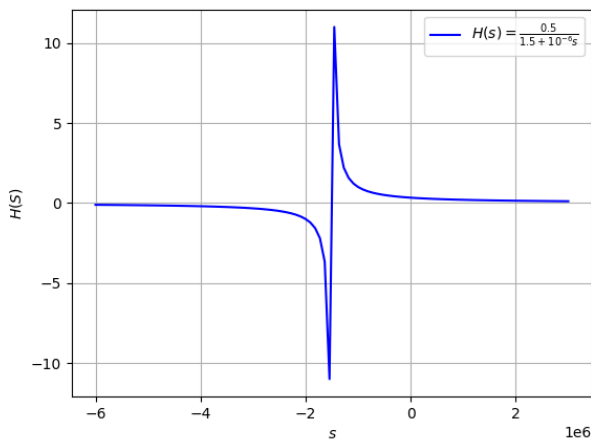


Fig. 4.1. Plot of  $H(s)$

Consider the frequency-domain transfer function by putting  $s = j\omega$

$$H(j\omega) = \frac{5 \times 10^5}{j\omega + 1.5 \times 10^6} \quad (4.9)$$

$$\Rightarrow |H(j\omega)| = \frac{5 \times 10^5}{\sqrt{\omega^2 + 2.25 \times 10^{12}}} \quad (4.10)$$

As  $\omega$  increases,  $|H(j\omega)|$  decreases

In other words, the amplitude of high-frequency signals gets diminished and they get filtered out

Therefore, this is a low-pass filter

4.4. Using trapezoidal rule for integration, formulate the difference equation by considering

$$y(n) = y(t)|_{t=n} \quad (4.11)$$

**Solution:**

$$\frac{v_c(t)}{R_1} + \frac{v_c(t) - v_2(t)}{R_2} + C_0 \frac{dv_c}{dt} = 0 \quad (4.12)$$

$$\Rightarrow C_0 \frac{dv_c}{dt} = \frac{2u(t) - v_c(t)}{R_2} - \frac{v_c(t)}{R_1} \quad (4.13)$$

$$\Rightarrow v_c(t)|_{t=n}^{n+1} = \int_n^{n+1} \left( \frac{2u(t) - v_c(t)}{R_2 C_0} - \frac{v_c(t)}{R_1 C_0} \right) dt \quad (4.14)$$

By the trapezoidal rule of integration

$$\int_a^b f(t) dt \approx \frac{b-a}{2} (f(a) + f(b)) \quad (4.15)$$

Consider  $y(t) = v_c(t)$

$$y(n+1) - y(n) = \frac{1}{R_2 C_0} (u(n) + u(n+1)) - \frac{1}{2} (y(n+1) + y(n)) \left( \frac{1}{R_1 C_0} + \frac{1}{R_2 C_0} \right) \quad (4.16)$$

Thus, the difference equation is

$$\begin{aligned} y(n+1) & \left( 1 + \frac{1}{2R_1 C_0} + \frac{1}{2R_2 C_0} \right) \\ &= y(n) \left( 1 - \frac{1}{2R_1 C_0} - \frac{1}{2R_2 C_0} \right) \\ & \quad + \frac{1}{R_2 C_0} (u(n) + u(n+1)) \end{aligned} \quad (4.17)$$

4.5. Find  $H(z)$

**Solution:** Let  $\mathcal{Z}\{y(n)\} = Y(z)$

On taking the Z-transform on both sides of the difference equation

$$\begin{aligned} zY(z) & \left( 1 + \frac{1}{2R_1 C_0} + \frac{1}{2R_2 C_0} \right) \\ &= Y(z) \left( 1 - \frac{1}{2R_1 C_0} - \frac{1}{2R_2 C_0} \right) \\ & \quad + \frac{1}{R_2 C_0} \left( \frac{1}{1-z^{-1}} + \frac{z}{1-z^{-1}} \right) \end{aligned} \quad (4.18)$$

$$\begin{aligned} Y(z) & \left( z + \frac{z}{2R_1 C_0} + \frac{z}{2R_2 C_0} - 1 + \frac{1}{2R_1 C_0} + \frac{1}{2R_2 C_0} \right) \\ &= \frac{1}{R_2 C_0} \frac{1+z}{1-z^{-1}} \end{aligned} \quad (4.19)$$

Also

$$v_2(t) = 2 \quad \forall t \geq 0 \quad (4.20)$$

$$\Rightarrow x(n) = 2u(n) \quad (4.21)$$

$$\Rightarrow X(z) = \frac{2}{1-z^{-1}} \quad |z| > 1 \quad (4.22)$$

Thus, the transfer function in  $z$ -domain is

$$H(z) = \frac{Y(z)}{X(z)} \quad (4.23)$$

$$= \frac{\frac{1+z}{2R_2C_0}}{z + \frac{z}{2R_1C_0} + \frac{z}{2R_2C_0} - 1 + \frac{1}{2R_1C_0} + \frac{1}{2R_2C_0}} \quad (4.24)$$

$$= \frac{\frac{1+z^{-1}}{2R_2C_0}}{1 + \frac{1}{2R_1C_0} + \frac{1}{2R_2C_0} - z^{-1} + \frac{z^{-1}}{2R_1C_0} + \frac{z^{-1}}{2R_2C_0}} \quad (4.25)$$

On substituting the values

$$H(z) = \frac{2.5 \times 10^5(1 + z^{-1})}{7.5 \times 10^5 + 1 + (7.5 \times 10^5 - 1)z^{-1}} \quad (4.26)$$

with the ROC being

$$|z| > \max\left(1, \left|\frac{7.5 \times 10^5 - 1}{7.5 \times 10^5 + 1}\right|\right) \quad (4.27)$$

$$\Rightarrow |z| > 1 \quad (4.28)$$

4.6. How can you obtain  $H(z)$  from  $H(s)$ ?

**Solution:** The  $Z$ -transform can be obtained from the Laplace transform by the substitution

$$s = \frac{2}{T} \frac{1 - z^{-1}}{1 + z^{-1}} \quad (4.29)$$

where  $T$  is the step size of the trapezoidal rule (1 in our case)

This is known as the bilinear transform

Thus

$$H(z) = \frac{\frac{1}{R_2C_0}}{2\frac{1-z^{-1}}{1+z^{-1}} + \frac{1}{R_1C_0} + \frac{1}{R_2C_0}} \quad (4.30)$$

$$= \frac{\frac{1+z^{-1}}{2R_2C_0}}{1 - z^{-1} + \left(\frac{1}{2R_1C_0} + \frac{1}{2R_2C_0}\right)(1 + z^{-1})} \quad (4.31)$$

$$= \frac{\frac{1+z^{-1}}{2R_2C_0}}{1 + \frac{1}{2R_1C_0} + \frac{1}{2R_2C_0} - z^{-1} + \frac{z^{-1}}{2R_1C_0} + \frac{z^{-1}}{2R_2C_0}} \quad (4.32)$$

$$= \frac{2.5 \times 10^5(1 + z^{-1})}{7.5 \times 10^5 + 1 + (7.5 \times 10^5 - 1)z^{-1}} \quad (4.33)$$

which is the same as what we obtained earlier

4.7. Find  $y(n)$  from  $H(z)$  and verify whether  $y(n) = y(t)|_{t=n}$

**Solution:**

$$Y(z) = H(z)X(z) \quad (4.34)$$

$$= \frac{2.5 \times 10^5(1 + z^{-1})}{7.5 \times 10^5 + 1 + (7.5 \times 10^5 - 1)z^{-1}} \frac{2}{1 - z^{-1}} \quad (4.35)$$

$$= \frac{\frac{2}{3}}{1 - z^{-1}} - \frac{\frac{2}{3}}{7.5 \times 10^5 + 1 + (7.5 \times 10^5 - 1)z^{-1}} \quad (4.36)$$

On taking the inverse  $Z$ -transform by considering the ROC to be  $|z| > 1$ , we get

$$y(n) = \frac{2}{3}u(n) - \frac{2}{3} \frac{1}{7.5 \times 10^5 + 1} \left( -\frac{7.5 \times 10^5 - 1}{7.5 \times 10^5 + 1} \right)^n u(n) \quad (4.37)$$

$$= \frac{2}{3} \left( 1 - \frac{(1 - 7.5 \times 10^5)^n}{(1 + 7.5 \times 10^5)^{n+1}} \right) u(n) \quad (4.38)$$

If we are sampling the signal at intervals of  $T \ll 10^{-5}$ , say `[parse-numbers = false]` $10^{-7}$ , i.e.,  $n = 10^{-7}, 2 \times 10^{-7}, \dots$

$$y(n) \approx \frac{2}{3} \left( 1 - \frac{1 - 7.5 \times 10^5 n}{1 + 7.5 \times 10^5 n} \right) u(n) \quad (4.39)$$

Now

$$Y(s) = H(s)X(s) \quad (4.40)$$

$$= \frac{5 \times 10^5}{s + 1.5 \times 10^6} \frac{2}{s} \quad (4.41)$$

$$= \frac{10^6}{1.5 \times 10^6} \left( \frac{1}{s} - \frac{1}{s + 1.5 \times 10^6} \right) \quad (4.42)$$

On taking the inverse Laplace transform by considering the ROC to be  $\Re(s) > 0$ , we get

$$y(t) = \frac{2}{3} \left( 1 - e^{-1.5 \times 10^6 t} \right) u(t) \quad (4.43)$$

But

$$e^{-1.5 \times 10^6 t} = \frac{e^{-0.75 \times 10^6 t}}{e^{0.75 \times 10^6 t}} \quad (4.44)$$

$$\approx \frac{1 - 7.5 \times 10^5 t}{1 + 7.5 \times 10^5 t} \quad \text{when } t \ll 10^{-6} \quad (4.45)$$

Therefore

$$y(t) \approx \frac{2}{3} \left( 1 - \frac{1 - 7.5 \times 10^5 t}{1 + 7.5 \times 10^5 t} \right) u(t) \quad (4.46)$$

$$\therefore y(n) = y(t)|_{t=n} \quad (4.47)$$

Download the following codes for simulation and plotting Fig. ?? respectively

```
wget https://github.com/AvinashNayak27/
  Spice/blob/master/codes/4.7.cir
wget https://github.com/AvinashNayak27/
  Spice/blob/master/codes/4.7.py
```

Run the codes by executing

```
ngspice 4.7.cir
python 4.7.py
```

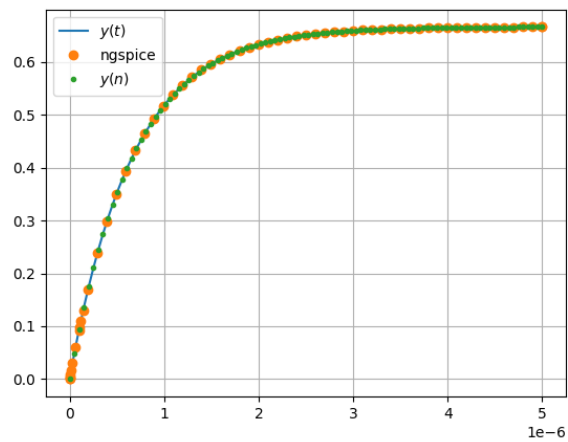


Fig. 4.2. Plots of  $y(t)$  and  $y(n)$